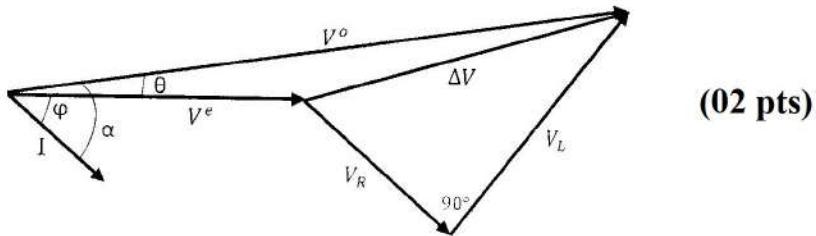


## Corrigé EMD RE

### Exercice 01: (12 pts)

#### 1- Le diagramme de Fresnel de la ligne :



#### 2- La tension de départ :

$$\overline{V^o} = \overline{V^e} + \bar{I} \times \bar{Z}$$

$$\overline{V^e} = 33000 \angle 0^\circ$$

$$\bar{I} = I \times (\cos \varphi - j \sin \varphi)$$

$$I = \frac{P^e}{V \times \cos \varphi} = \frac{1100 \times 10^3}{33000 \times 0.8} = 41.67 \text{ A}$$

$$\cos \varphi = 0.8 \quad \sin \varphi = 0.6$$

$$\bar{I} = 41.67 \times (0.8 - j0.6) = 33.33 - j25$$

$$\bar{I} = A + jB = C \angle \varphi^\circ = C e^{+j\theta} \quad \text{avec } C = \sqrt{A^2 + B^2} \text{ et } \varphi = \arg \frac{B}{A}$$

$$C = \sqrt{A^2 + B^2} = \sqrt{33.33^2 + 25^2} = 41.67$$

$$\varphi = \arg \frac{B}{A} = \arg \frac{25}{33.33} = \arg 0.75 = 36.87^\circ$$

$$\bar{I} = 33.33 - j25 = 41.67 \angle 36.87^\circ = 41.67 e^{-j36.87}$$

$$\overline{V^o} = \overline{V^e} + \bar{I} \times \bar{Z} = 33000 + (33.33 - j25) \times (10 + j15) = 33708.3 + j249.95$$

$$C = \sqrt{33708.3^2 + 249.95^2} = 33709.22$$

$$\theta = \arg \frac{249.95}{33708.3} = \arg 0.0074 = 0.42^\circ$$

$$\overline{V^o} = 33709.22 \angle 0.42^\circ = 33709.22 e^{+j0.42^\circ} \quad \text{(03 pts)}$$

## **Le facteur de puissance de départ :**

$$\text{Le facteur de puissance} = \cos \alpha \quad \text{avec } \alpha = \varphi + \theta$$

$$\alpha = 36.87 + 0.42 = 37.29^\circ$$

$$FP = \cos 37.29^\circ = 0.79 \quad \textbf{(03 pts)}$$

## **3- Les pertes en ligne :**

$$\Delta P = R \times I^2 = 10 \times 41.67^2 = 17.364 \text{ kW} \quad \textbf{(01 pts)}$$

$$\Delta Q = X \times I^2 = 15 \times 41.67^2 = 26.046 \text{ kVAR} \quad \textbf{(01 pts)}$$

## **Le rendement de la ligne :**

$$\eta = \frac{P^e}{P^o} = \frac{P^e}{P^e + \Delta P} = \frac{1100 \times 10^3}{1100 \times 10^3 + 17.364 \times 10^3} = 0.98 \quad \textbf{(02 pts)}$$

**Exercice 02 : (08 pts)**

**Question de cours.**