

**TD N°2.2:\***

**Exercice N° 04**

- a- Consider an RL circuit whose effective current is  $I=1A$ .  $R=100\Omega$ ,  $L=38.6mH$ ,  $f=50Hz$ . Determine the effective values  $U_R$ ,  $U_L$  and  $U_t$  and the corresponding phase shift.
- b- Consider an RC circuit whose effective current is  $I= 1A$ .  $R=100\Omega$ ,  $C=35\mu F$ ,  $f=50Hz$ . Determine the effective values de  $U_R$ ,  $U_C$  et  $U_t$  and the corresponding phase shift.

**Exercice N° 05**

A  $25 \Omega$  resistor, a  $10 \mu F$  capacitor and a  $0.1H$  inductor which has an internal resistance of  $12 \Omega$  are connected in series. Determine for a frequency of  $50 Hz$ :

1. The coil impedance and the capacitor impedance.
2. The module of the overall circuit impedance.
3. What is the nature of the charge.
4. Calculate the effective current in the circuit for a sinusoidal voltage of maximum value  $300 V$ .

**Exercice N° 06**

We consider the circuit represented in the figure where is the complex representation of a sinusoidal voltage with effective value  $V=100 V$  and frequency  $50 Hz$ . The components of this circuit are directly characterized by the value of their complex impedance.


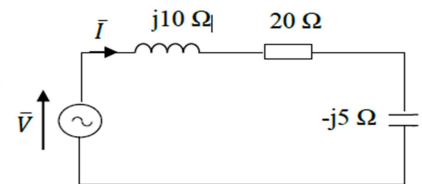


Figure 1

1. Calculate the effective value  $I$  of the current.
2. Calculate the phase of the current if we consider the voltage at the origin of the phases. Then write the time expression for the voltage  $v(t)$  and the current  $i(t)$ .
3. Represent all the complexes forming this mesh law on a vector diagram in the complex plane (Fresnel diagram).

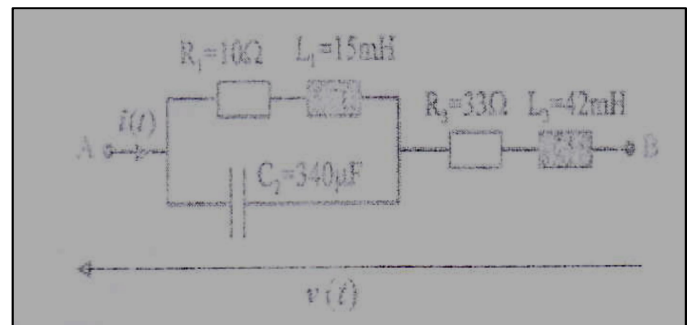**Exercice N° 07**


Calculate the impedances of each branch and the equivalent impedance and the current  $i(t)$ , Knowing that  $V(t)= 220 \sqrt{2}\sin 314t$ .




**Exercice N° 08 (homework to do at home and return)**

For the following three circuits, determine:

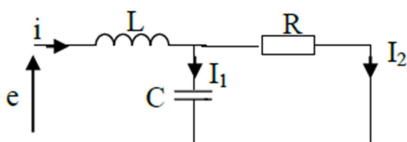
1. Their complex impedance.
  2. Intensities  $i$  and  $i_1$
- A. N For a sinusoidal voltage of maximum value  $10 V$  ;  $R = 2\Omega$ ,  $C = 10\mu F$ ,  $L 5\mu H$ .



-A

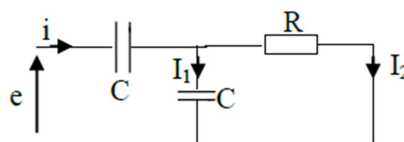

-B

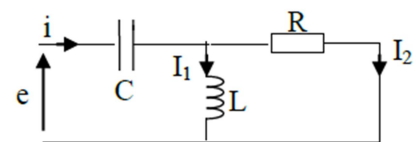

-C