



Chapter 4: Boolean Algebra and Combinational circuits

Dr. Khelifi Hakima

S1- 2025/2026

Lessons Objectives

- ✓ Definition
- ✓ Fundamental concepts
- ✓ Laws of the Boolean Algebra
- ✓ Truth table and Logic gates
- ✓ Design steps of a combinational circuit

Definition

Definition

- Boolean algebra was introduced in 1847 by Georges Boole.
- It is a branch of mathematics that deals with operations on logical values with binary variables.
- These variables are represented as binary numbers to represent truths: 1 = true and 0 = false.
- It forms the basis for designing digital circuits and performing logical operations.

Fundamental concepts

Fundamental concepts

- **State:** Logical states are represented by 0 and 1.
- **Boolean variable:** can take one of two possible values: 0 or 1, representing false and true. These variables are used in Boolean algebra to represent logical statements or conditions.
- **Boolean function:** is an expression formed using Boolean variables, constants (0 or 1), and logical operations (AND, OR, NOT, etc.). There are two types of operator:
 - ✓ **Basic operators:** NOT, AND, OR
 - ✓ **Derived operators:** NOT-AND (NAND) , NOT OR (NOR), Exclusive OR (XOR), Not Exclusive OR (NXOR).

Laws of the Boolean Algebra

Laws of the Boolean Algebra

➤ Identity Law :

✓ **AND:** $A \cdot 1 = A$ (AND with 1 leaves the variable unchanged)

✓ **OR:** $A + 0 = A$ (OR with 0 leaves the variable unchanged)

➤ Commutative Law: operating Boolean variables A and B is similar to operating Boolean variables B and A

✓ **AND:** $A \cdot B = B \cdot A$

✓ **OR:** $A + B = B + A$

➤ Associative Law: the order of performing Boolean operator is illogical as their result is always the same

✓ **AND:** $A \cdot (B \cdot C) = (A \cdot B) \cdot C$

✓ **OR:** $A + (B + C) = (A + B) + C$

Laws of the Boolean Algebra

- **Distributive Law** : AND distributes over OR, and OR distributes over AND
 - ✓ **AND over OR**: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$
 - ✓ **OR over AND**: $A + (B \cdot C) = (A + B) \cdot (A + C)$
- ✓ **Inversion Law**: the complement of the complement of any number is the number itself. Also, A variable ANDed with its complement is 0, and ORed with its complement is 1
 - ✓ $\overline{\overline{A}} = A$
 - ✓ **AND**: $A \cdot \overline{A} = 0$
 - ✓ **OR**: $A + \overline{A} = 1$
- **Null Law**: Multiplying by 0 always gives 0, adding 1 always gives 1
 - ✓ **AND**: $A \cdot 0 = 0$
 - ✓ **OR**: $A + 1 = 1$

Laws of the Boolean Algebra

➤ Absorption Law:

- ✓ $A \cdot (A + B) = A$ (A ANDed with the OR of A and B is just A)
- ✓ $A + (A \cdot B) = A$ (A ORed with the AND of A and B is just A)

➤ MORGAN'S LAW:

1. The complement of the product (AND) of two Boolean variables is equal to the sum (OR) of the complement of each Boolean variable: $\overline{A \cdot B} = \overline{A} + \overline{B}$
2. The Complement of the sum (OR) of two Boolean variables is equal to the product(AND) of the complement of each Boolean variable: $\overline{A + B} = \overline{A} \cdot \overline{B}$

Laws of the Boolean Algebra

➤ **Example 1:** $A \cdot (B+C) + A \cdot \bar{C}$

✓ **Distributive Law:** $A \cdot B + A \cdot C + A \cdot \bar{C}$

✓ **Inversion Law:** $A \cdot C + A \cdot \bar{C} = A \cdot (C + \bar{C}) = A \cdot 1$

✓ **Identity Law:** $A \cdot 1 = A$

✓ **Absorption Law:** $A \cdot (B+A) = A$

✓ **Final simplified expression** = A

Truth table and Logic gates

Truth table and Logic gates

- Logic gate is a fundamental building block of digital circuits.
- It performs a basic logical function on one or more binary inputs to produce a single output.
- Based on the logic operation it carries out, the output is typically a binary value (0 or 1).
- There are several common types of logic gates: **NOT, AND, OR, NOT-AND (NAND) , NOT OR (NOR), Exclusive OR (XOR), Not Exclusive OR (NXOR).**

Truth table and Logic gates

- Logic functions can be represented by truth tables. The truth table shows the output of a logic circuit as a function of the various combinations of input values.
- The number of columns is the total number of inputs and outputs
- The number of rows is 2^N , where "N" is the number of inputs
- The value of a logic function is equal to 1 or 0, depending on the values of the logic variables.

Truth table and Logic gates


- A function with 3 inputs and 1 output is represented by a table with 4 columns and 8 rows.

A	B	C	Result
0	0	0	$\bar{A} \bar{B} \bar{C}$
0	0	1	$\bar{A} \bar{B} C$
0	1	0	$\bar{A} B \bar{C}$
0	1	1	$\bar{A} B C$
1	0	0	$A \bar{B} \bar{C}$
1	0	1	$A \bar{B} C$
1	1	0	$A B \bar{C}$
1	1	1	$A B C$

Truth table and Logic gates

- The seven basic logic gates are **AND, OR, NOR, XOR, NOT, NAND, and NXOR**.
- **LOGICAL FUNCTION (NOT): $F = \overline{A}$**

A	F
0	1
1	0

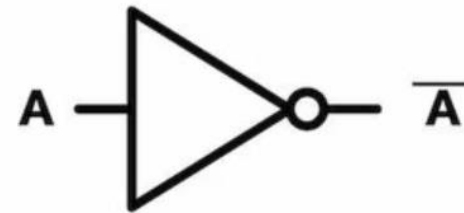

Truth table and Logic gates

➤ The seven basic logic gates are **AND, OR, NOR, XOR, NOT, NAND, and XNOR**.


➤ **LOGICAL FUNCTION AND:** $F = A * B$ ou $A \cdot B$ ou AB

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1



➤ **LOGICAL FUNCTION NOT AND (NAND):** $F = A/B$ ou $\overline{A \cdot B}$


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

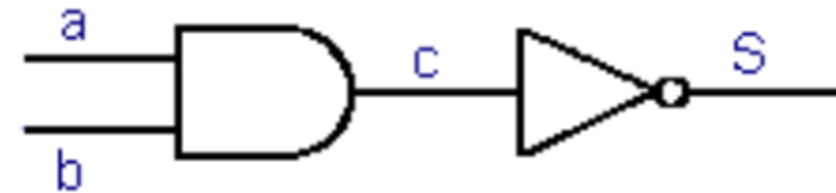

Truth table and Logic gates



➤ LOGICAL FUNCTION OR: $F = A + B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

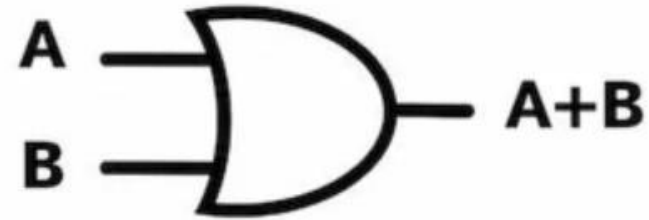

➤ LOGICAL FUNCTION NOT OR(NOR): $F = \overline{A + B}$


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

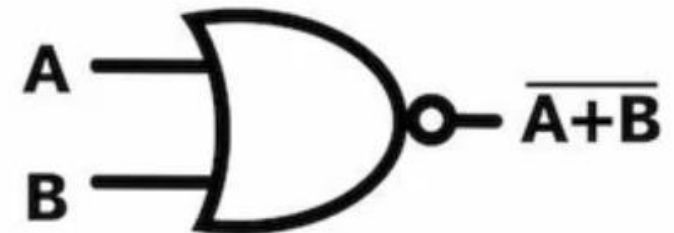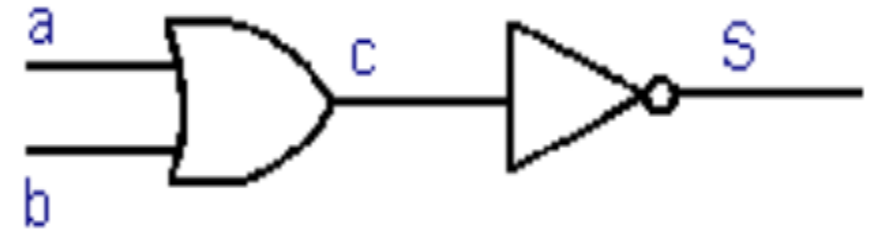

Truth table and Logic gates


➤ LOGICAL FUNCTION XOR (EXCLUSIVE OR): $F = A \oplus B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

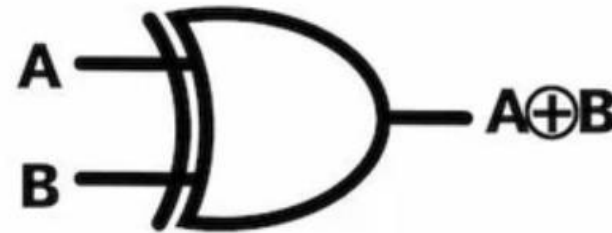

➤ LOGICAL FUNCTION NXOR: $F = \overline{A \oplus B}$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

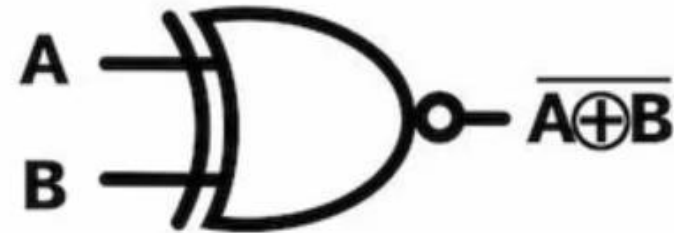

Truth table and Logic gates

➤ Example: $F(A, B) = (A \cdot \overline{B}) + (A + B)$

A	B	$\overline{B}$	$A \cdot \overline{B}$	$A + B$	$F(A, B) = (A \cdot \overline{B}) + (A + B)$
0	0	1	0	0	0
0	1	0	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1

Design steps of a combinational circuit

Design steps of a combinational circuit

- A combinational circuit is a digital circuit in which the output depends on the present input values.
- It is essentially a mapping from input values to output values based purely on Boolean algebra.
- It is an assembly of logic gates linked together to represent an algebraic expression.
- combinational circuits are used to create other, more complex circuits.

Design steps of a combinational circuit

➤ Components of a Combinational Circuit:

1. **Logic Gates:** The basic building blocks (AND, OR, NOT, NAND, NOR, XOR, NXOR).
2. **Input:** The variables fed into the circuit.
3. **Output:** The result after processing the inputs with logical operations.
4. **Interconnections:** Wires or connections that link the gates and inputs to outputs.

Design steps of a combinational circuit

- Steps to design a combinational circuit:
- ✓ **Define the Problem:** understand the requirements of the circuit, including what the inputs and outputs represent and the relationship between them.
- ✓ **Obtain Truth Table:** create a truth table that shows all possible combinations of input values and the corresponding output values.
- ✓ **Simplify the Boolean Expression:** can use Boolean algebra to simplify the expressions.
- ✓ **Select Logic Gates:** Based on the simplified Boolean expressions, choose the appropriate logic gates (AND, OR, NOT, NAND, NOR, XOR, etc.) to implement the circuit.
- ✓ **Draw the Circuit Diagram:** use standard symbols for gates and connect the inputs, gates, and outputs.

Design steps of a combinational circuit

➤ Steps to design a combinational circuit:

➤ **Example: Full Adder circuit**

✓ **Define the Problem:** A Full Adder takes three binary inputs: **A**, **B** (the two data bits), and C_{in} (carry input). It produces two outputs: the **sum (S)** and the carry output (C_{out}).

✓ **Obtain Truth Table:**

A	B	C_{in}	sum (S)	Carry (C_{out})
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Design steps of a combinational circuit

➤ Steps to design a combinational circuit:

➤ Example: Full Adder circuit

✓ Simplify the Boolean Expression :

- **Sum (S):** The sum can be represented by the XOR operation: $S = A \oplus B \oplus C_{in}$
- **Carry (C_{out}):** The carry output is generated by the following OR and AND operations:
 $C_{out} = (A \cdot B) + (B \cdot C_{in}) + (A \cdot C_{in})$


A	B	C_{in}	sum (S)	Carry (C_{out})	$A \oplus B$	$A \oplus B \oplus C_{in}$	$A \cdot B$	$B \cdot C_{in}$	$A \cdot C_{in}$
0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	1	0	0	0
0	1	0	1	0	1	1	0	0	0
0	1	1	0	1	1	0	0	1	0
1	0	0	1	0	1	1	0	0	0
1	0	1	0	1	1	0	0	0	1
1	1	0	0	1	0	0	1	0	0
1	1	1	1	1	0	1	1	1	1

Design steps of a combinational circuit

- Steps to design a combinational circuit:
- **Example: Full Adder circuit**
- ✓ **Select Logic Gates:**
- ✓ For the sum (S), use two XOR gates: First XOR gate for $A \oplus B$, Second XOR gate for $(A \oplus B) \oplus C_{in}$.
- ✓ For the carry (C_{out}), use three AND gates and one OR gate:
 - ✓ Three AND gates to compute $A \cdot B$, $B \cdot C_{in}$, and $A \cdot C_{in}$,
 - ✓ One OR gate to combine these AND outputs.


Design steps of a combinational circuit

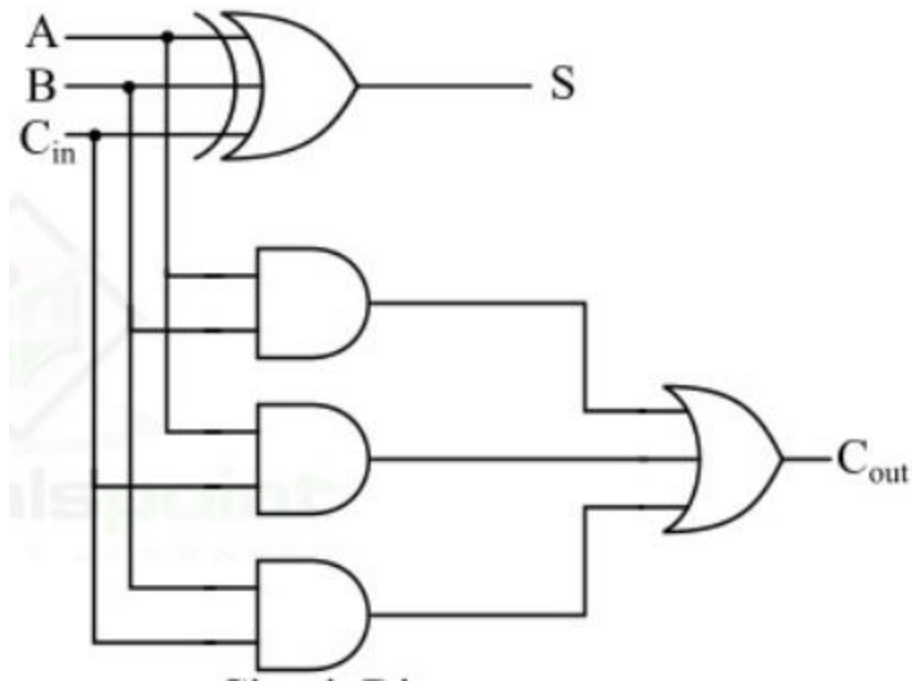- Steps to design a combinational circuit:
- **Example: Full Adder circuit**
- ✓ **Draw the Circuit Diagram:**



Design steps of a combinational circuit

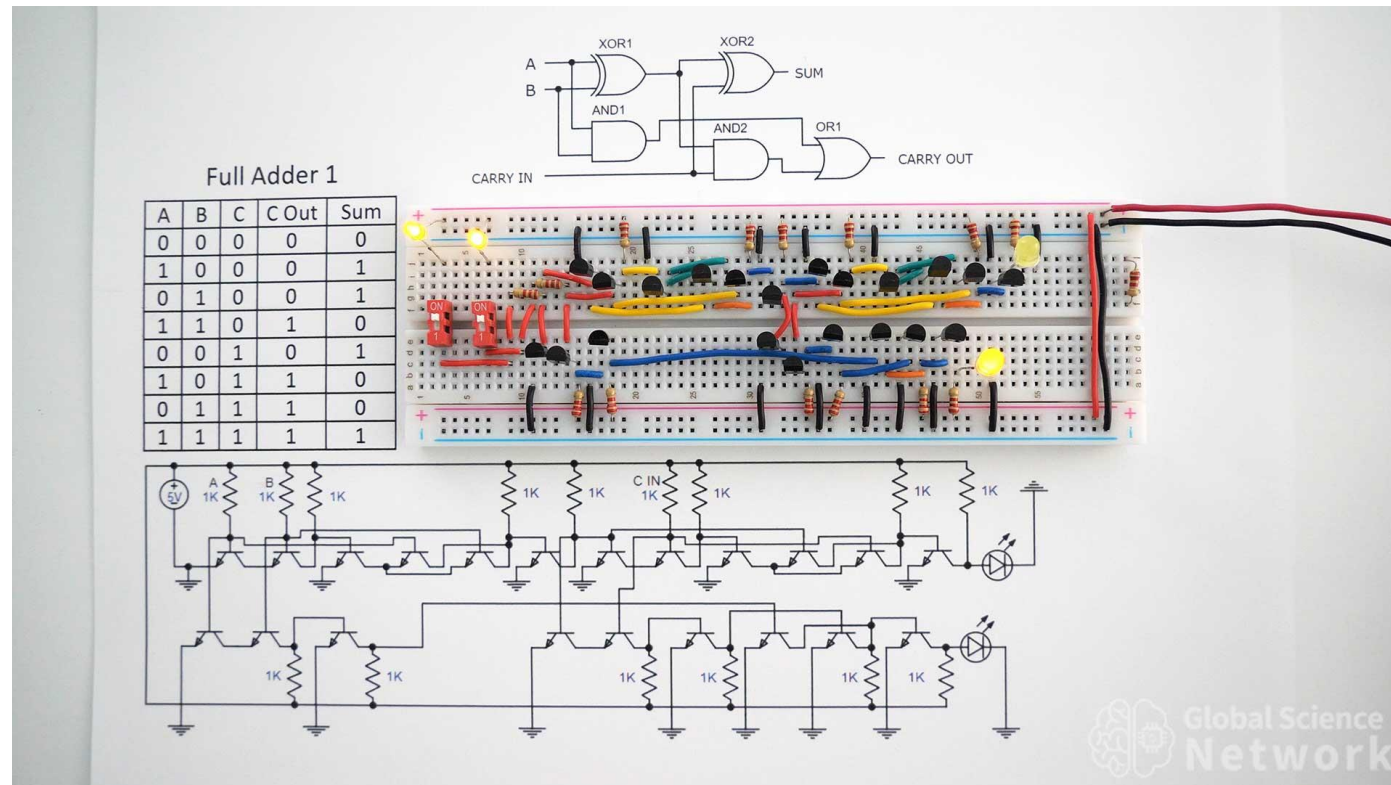- Steps to design a combinational circuit:
- **Example: Full Adder circuit**
- ✓ **Draw the Circuit Diagram:**



The end